

# Lab 7


## Objectives

To construct and study the function of the volume unit meter (VU Meter).

### Vout1-pp



### Vout2-pp

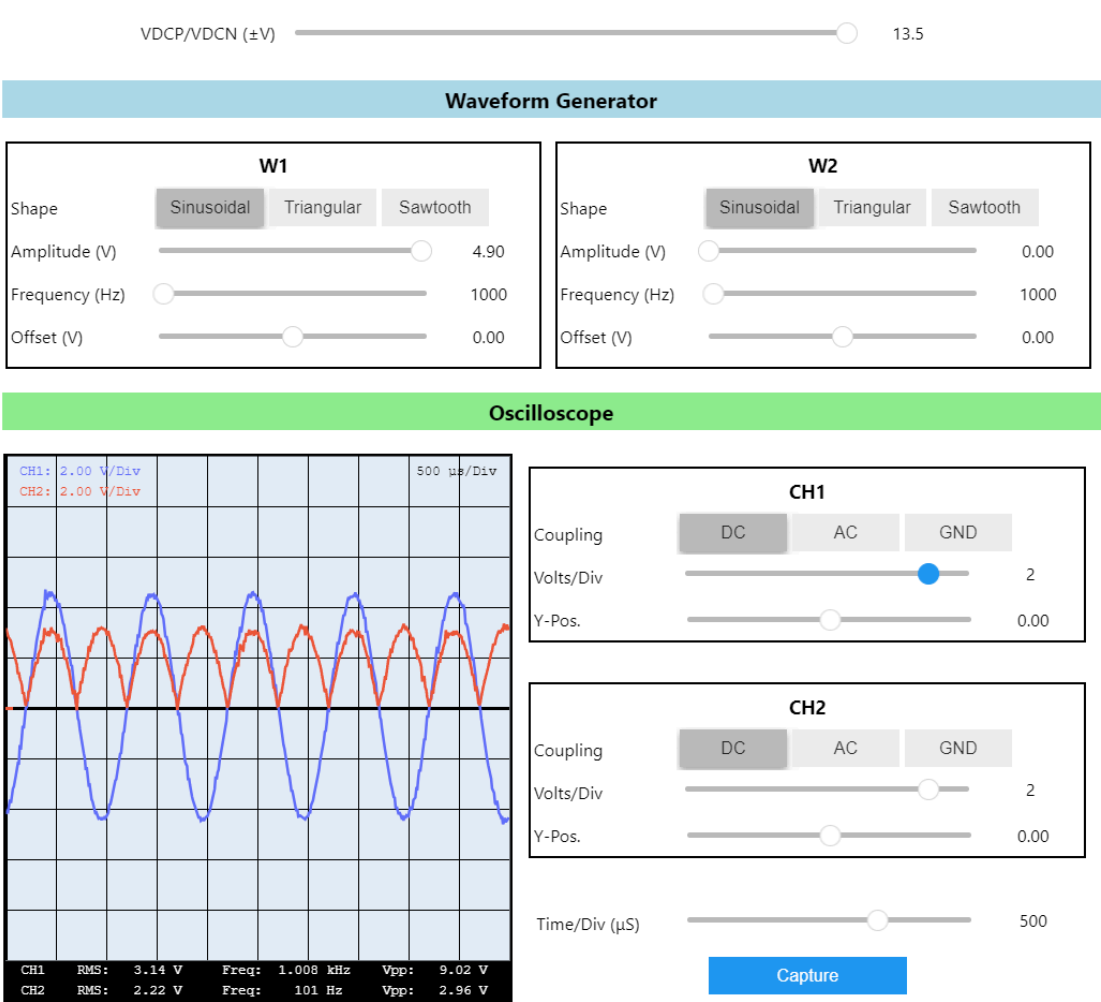


VDCP/VDCN ( $\pm$ V)

13.5

## Waveform Generator

W1		W2	
Shape	<input checked="" type="radio"/> Sinusoidal <input type="radio"/> Triangular <input type="radio"/> Sawtooth	Shape	<input checked="" type="radio"/> Sinusoidal <input type="radio"/> Triangular <input type="radio"/> Sawtooth
Amplitude (V)	<input type="range"/> 4.90	Amplitude (V)	<input type="range"/> 0.00
Frequency (Hz)	<input type="range"/> 1000	Frequency (Hz)	<input type="range"/> 1000
Offset (V)	<input type="range"/> 0.00	Offset (V)	<input type="range"/> 0.00

## Oscilloscope

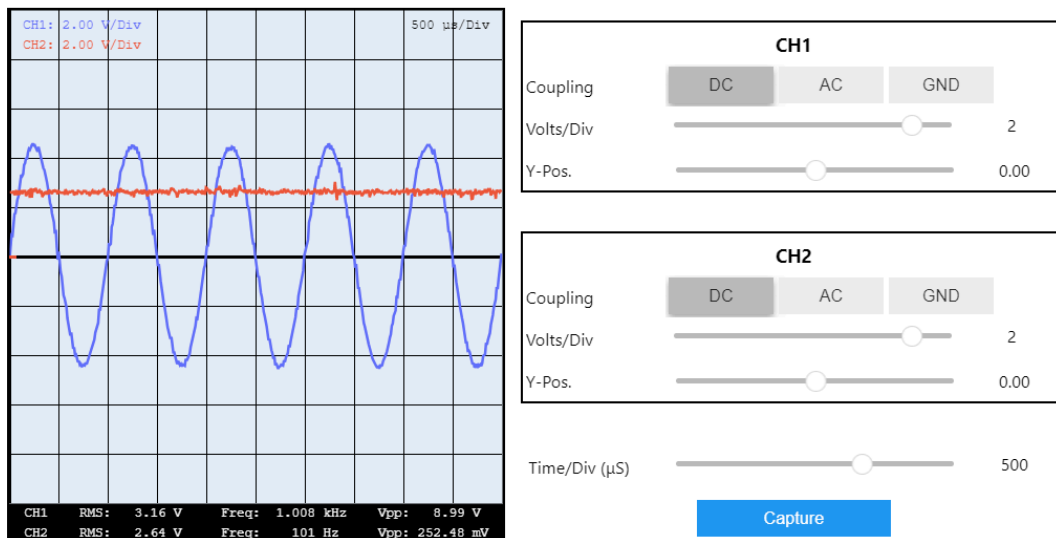

Amp(V)	Vin-pp(V)	Vo1-pp(V)	Vo2-pp(V)	Vo3-RMS(V)
4.9	8.98	3.84	3.1	2.64
3.8	7.02	3.2	2.34	1.96
3.9	7.18	3.28	2.43	2.02
2.8	5.2	2.56	1.74	1.36
2.9	5.26	2.5	1.76	1.32
1.8	3.46	1.9	1.2	753.9m
1.9	3.54	1.88	1.21	815.69m
0.8	1.56	1.22	643.63m	246.82m
0.9	1.76	1.27	655.72m	294.90m

## VU Meter gain measurement

## VU Meter gain characterization

```
In [ ]: import numpy as np
import plotly.graph_objs as go
from plotly.subplots import make_subplots
```

```


vpp_IN = np.array([8.98,7.02,7.18,5.2,5.26,3.46,3.54,1.56,1.76])
v_OUT_01 = np.array([3.84,3.2,3.28,2.56,2.5,1.9,1.88,1.22,1.27])
v_OUT_02 = np.array([3.1,2.34,2.43,1.74,1.76,1.2,1.21,0.64363,0.65572])
vrms_OUT_03 = np.array([2.64,1.96,2.02,1.36,1.32,0.7539,0.81569,0.24682,0.2949])

gain_v_OUT_02 = (2*v_OUT_02)/vpp_IN

fig = go.Figure()
#fig.update_xaxes(type='Log')
fig = make_subplots(specs=[[{"secondary_y": True}]]
fig.add_trace(go.Scatter(x=vpp_IN, y=gain_v_OUT_02, mode='markers', name='V<sub>OUT2</sub> Gain'))
fig.add_trace(go.Scatter(x=vpp_IN, y=vrms_OUT_03, mode='markers', name='V<sub>OUT3</sub> RMS'))
fig.update_xaxes(title_text="V<sub>IN</sub>-pp")
fig.update_yaxes(title_text="<b>primary</b> V<sub>OUT2</sub> Gain", secondary_y=
fig.update_yaxes(title_text="<b>secondary</b> V<sub>OUT3</sub> RMS", secondary_y=
#fig.update_layout(xaxis_title='V<sub>IN</sub>-pp', yaxis_title='V<sub>OUT3</sub>')

coef = np.polyfit(vpp_IN, gain_v_OUT_02, deg=1) # deg=1 for order 1 polynomial (
fit = coef[0]*vpp_IN + coef[1]
lab_temp = 25 # Laboratory temperature
fig.add_trace(go.Scatter(x=vpp_IN, y=fit, mode='lines', line=dict(dash='dash'),
name='Best fit for V<sub>OUT2</sub> Gain'))
coef = np.polyfit(vpp_IN, vrms_OUT_03, deg=1) # deg=1 for order 1 polynomial (li
fit = coef[0]*vpp_IN + coef[1]
lab_temp = 25 # Laboratory temperature
fig.add_trace(go.Scatter(x=vpp_IN, y=fit, mode='lines', line=dict(dash='dash'),
name='Best fit for V<sub>OUT3</sub> RMS'))

```

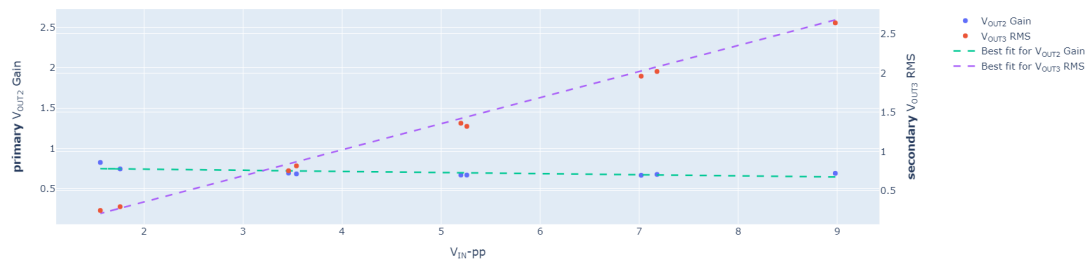

```

In [ ]: total_gain_out2 = 0.0
for i in range(len(gain_v_OUT_02)):
    total_gain_out2 += gain_v_OUT_02[i]

print("Average Gain (Vout2-pp)", total_gain_out2/9.0 )

```

Average Gain (Vout2-pp) 0.7022180900271009

The average gain from my measured values is around 0.702. This is very close to the theoretical gain value of 0.7

The function of a VU meter can be met as the the plot of Vout3/Vin produces a linear best fit line. Which indicates that the Vout3 follows Vin linearly.

## Open-Ended Questions

1. What do the two diodes do in the VU Meter? Explain using the waveforms observed at  $V_{OUT1}$  and  $V_{OUT2}$ .

ANS: The first diode acts as a full-wave rectifier. The second diode acts as a peak detector. Together with the capacitor, it detects and holds the peak voltage levels of the output.

2. What happens to  $V_{OUT3}$  if there is a DC offset at  $V_{IN}$ ?

ANS:  $V_{OUT3}$  will produce an inaccurate reading as the DC offset from the  $V_{in}$  will be amplified and cause the  $V_{out3}$  to change. Too high of a DC offset might cause damage to the amplifier.

3. At what volume, i.e., PA output amplitude, does the VU Meter fail to function?

ANS: From the voltage source of the op-amp, a volume that will cause the Op-amp to saturate to 13.5V will cause the Vu meter to fail as it is limited by the voltage source of the op amp.