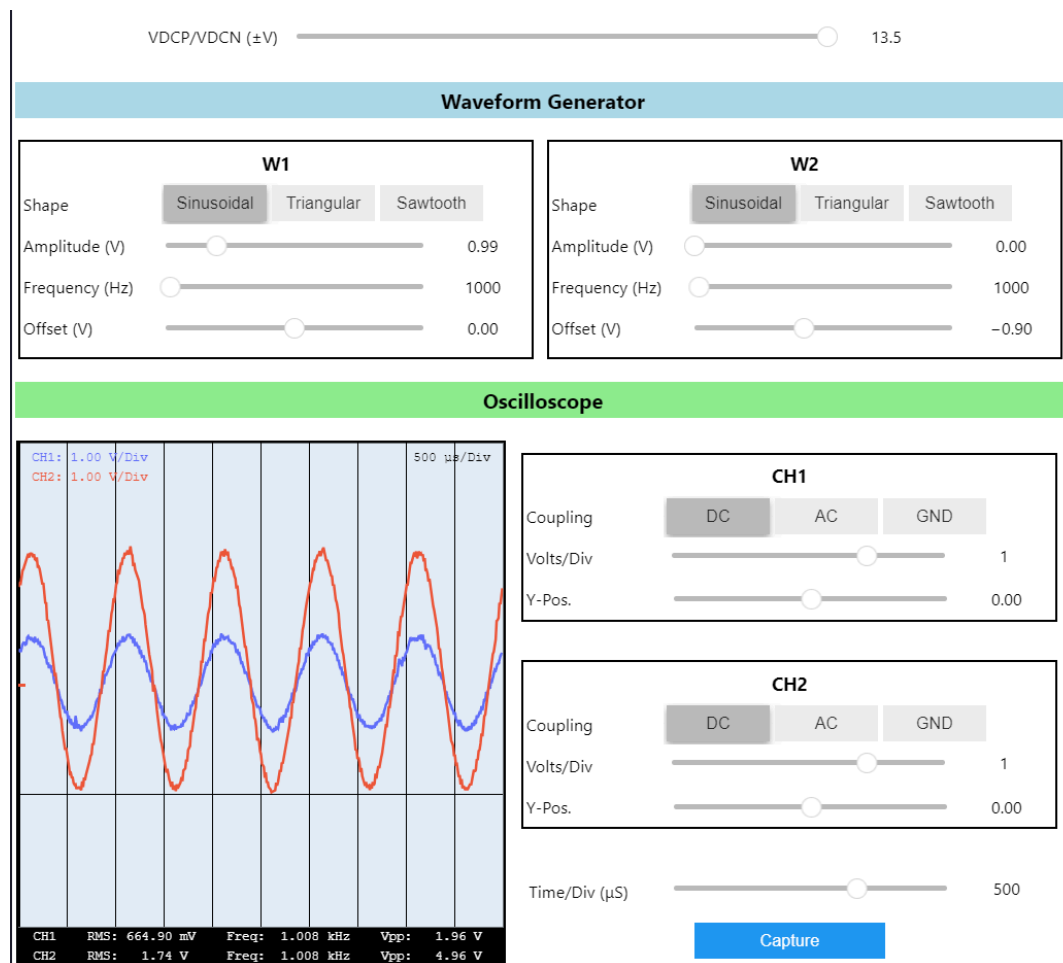


Lab 5

Objective

To construct and study the transfer characteristic of the voltage-controlled amplifier (VCA) subsystem.

Capture Example



```
In [ ]: #communication channel setup
import serial
import serial.tools.list_ports
import numpy as np
import plotly.graph_objs as go

VID = 61525
PID = 38912

device = None

ports = serial.tools.list_ports.comports()
for p in ports:
    if p.vid == VID and p.pid == PID:
        try:
```

```

        device = serial.Serial(p.device)
    except serial.SerialException:
        print('Reconnect the controller unit.')

if device is None:
    raise Exception('No suitable device detected.')

```

VCA gain characterization

```


In [ ]: import numpy as np
import plotly.graph_objs as go

v_a = np.array([5.4, 4.5, 3.6, 2.7, 1.8, 0.9, 0, -0.9, -1.8, -2.7])
v_IN = np.array([5.7, 5.48, 5.5, 5.5, 3.61, 3.63, 3.62, 1.96, 1.8, 1.7])
v_OUT = np.array([0.51, 0.55, 0.46, 0.66, 0.8, 1.8, 3.63, 4.91, 10.81, 24.18])

v_C = 3.3 / (56 + 3.3) * v_a # Eq. (5.2)
gain = 20 * np.log10(v_OUT / v_IN) # Eq. (5.3)

fig = go.Figure()
fig.add_trace(go.Scatter(x=v_C, y=gain, mode='markers', name='Measured gain'))
fig.update_layout(xaxis_title='V<sub>C</sub> (V)', yaxis_title='Gain (dB)')

```

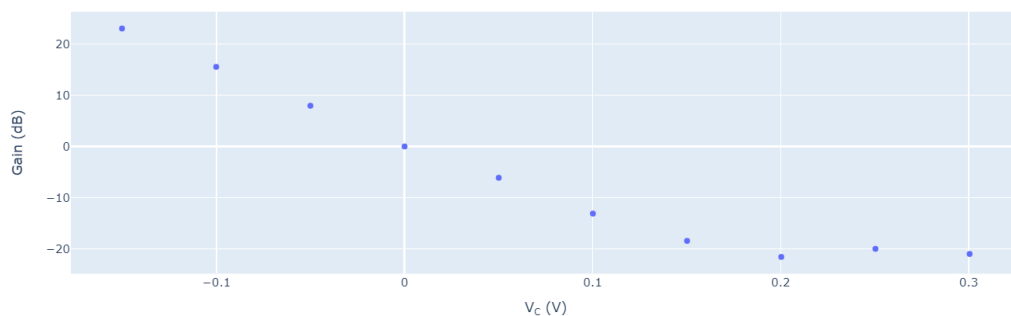

```

In [ ]: coef = np.polyfit(v_C, gain, deg=1) # deg=1 for order 1 polynomial (linear)
fit = coef[0]*v_C + coef[1]

lab_temp = 25 # Laboratory temperature
gain_spec = -v_C / (0.006 * (1 + 0.0033 * (lab_temp - 25))) # Eq. (5.1)


fig.add_trace(go.Scatter(x=v_C, y=fit, mode='lines', line=dict(dash='dash'),
    name='Best fit'))
fig.add_trace(go.Scatter(x=v_C, y=gain_spec, mode='lines', line=dict(dash='dot'),
    name='Specified gain'))

print('m = ' + str(coef[0]))
print('measured gain sensitivity = ' + str(1/coef[0]))

```

m = -103.4584811782203

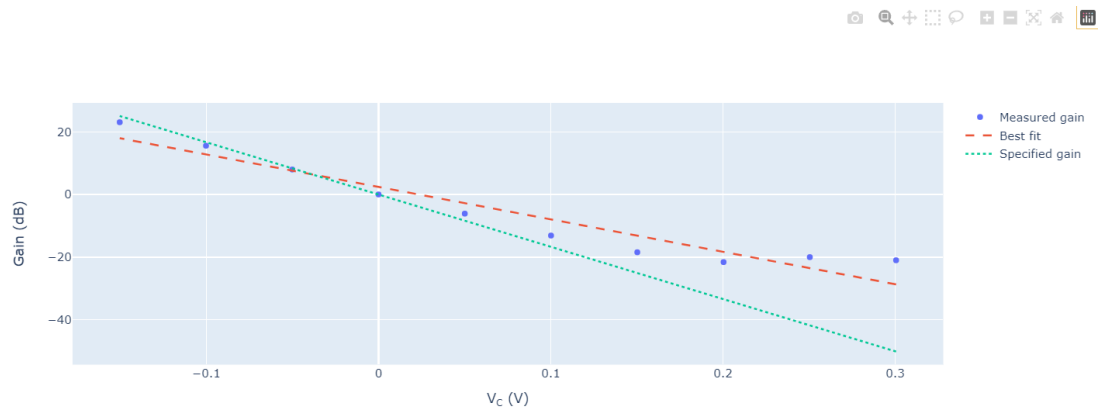measured gain sensitivity = -0.00966571313063618



Measured gain sensitivity = $\sim -9\text{mV/dB}$, which is larger in magnitude than the specified gain sensitivity

Applying small signal amplitude results in low V_{in} which also results in high V_{out}

High signal amplitude with high VCA gains will result in saturation which in theory let $V_{out} = +13.5\text{V} / -13.5\text{V}$

Open-Ended Questions

A VCA is a processor that can change the amplitude of a signal in response to a control voltage applied to its amplitude modulation control input.